

# Assignment 1

1	Explain classification of electrical networks	
2	Three resistances are connected in delta obtain the star equivalent of the circuit	
3	Obtain the equivalent resistance between any two points	
		